

PROPER CENTRE TAP RECTIFIER WITH RLC LOAD

PRESENTED BY -

Shubham faujdar

2023EEM1051

PRESENTED TO -

Dr C.C. Reddy

Professor

Head of the department

DEPARTMENT OF ELECTRICAL ENGINEERING
INDIAN INSTITUTE OF TECHNOLOGY ROPAR

SIMULATION IN LTSPICE

COMPONENTS FOR HARDWARE -

1) Diode = 1N4007

max. forward voltage drop = 1.1V

Max dc blocking voltage = 1000V


Forward current = 1A


2) Capacitor = 330 μ f, 63V

3) Inductor = 300 μ f


4) Resistance = 95k

5) Filter capacitor = 1 μ f, 63V

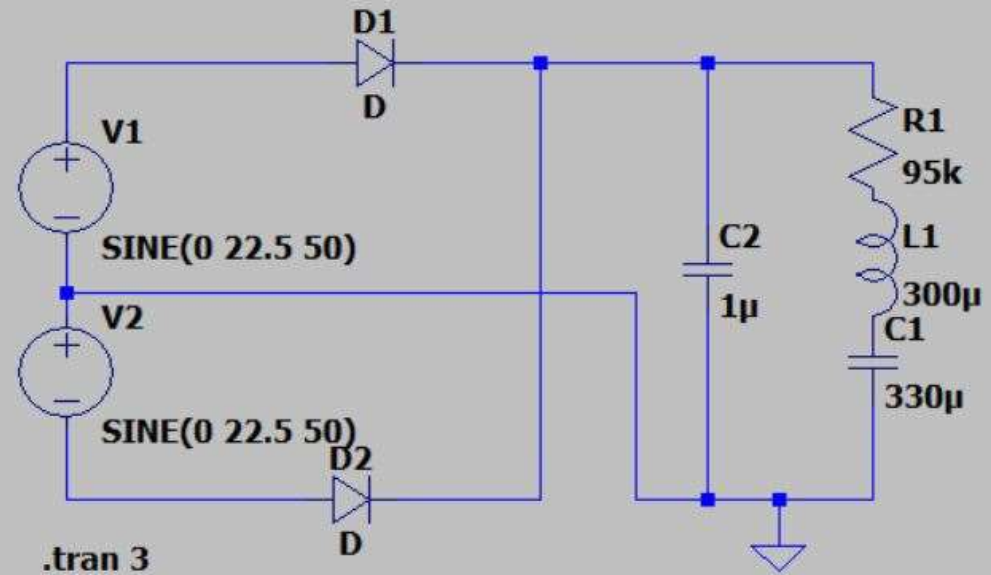

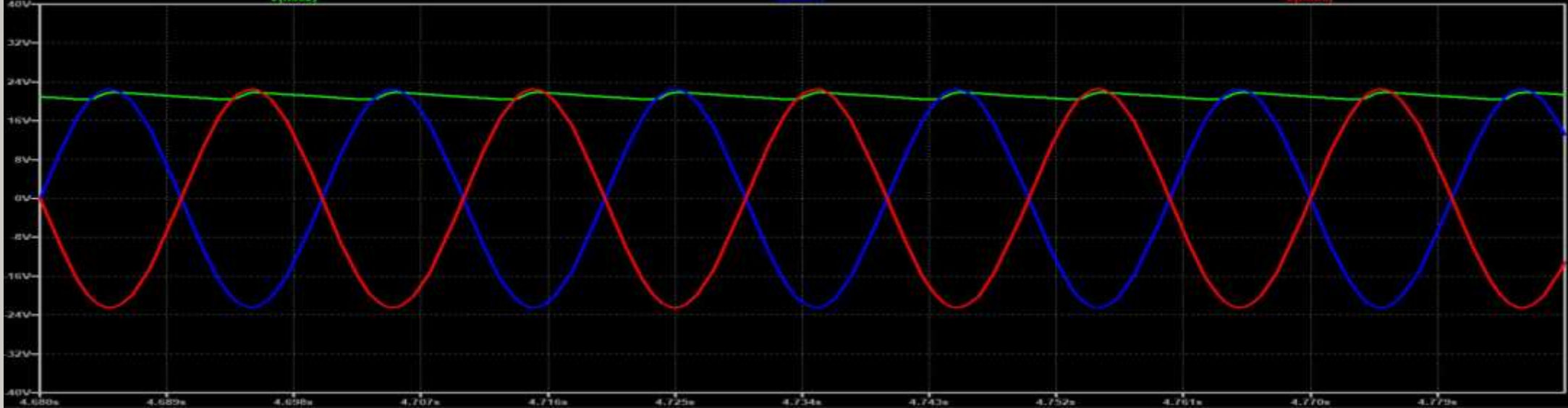


Simulation result in ItsPice

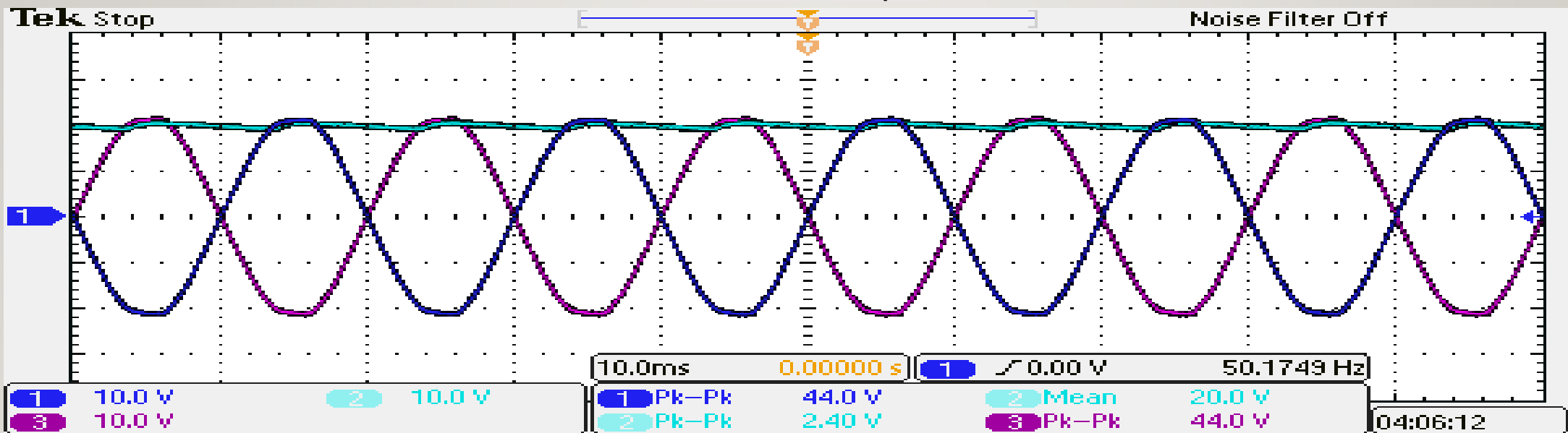

DSO result



Simulation result in Itspice

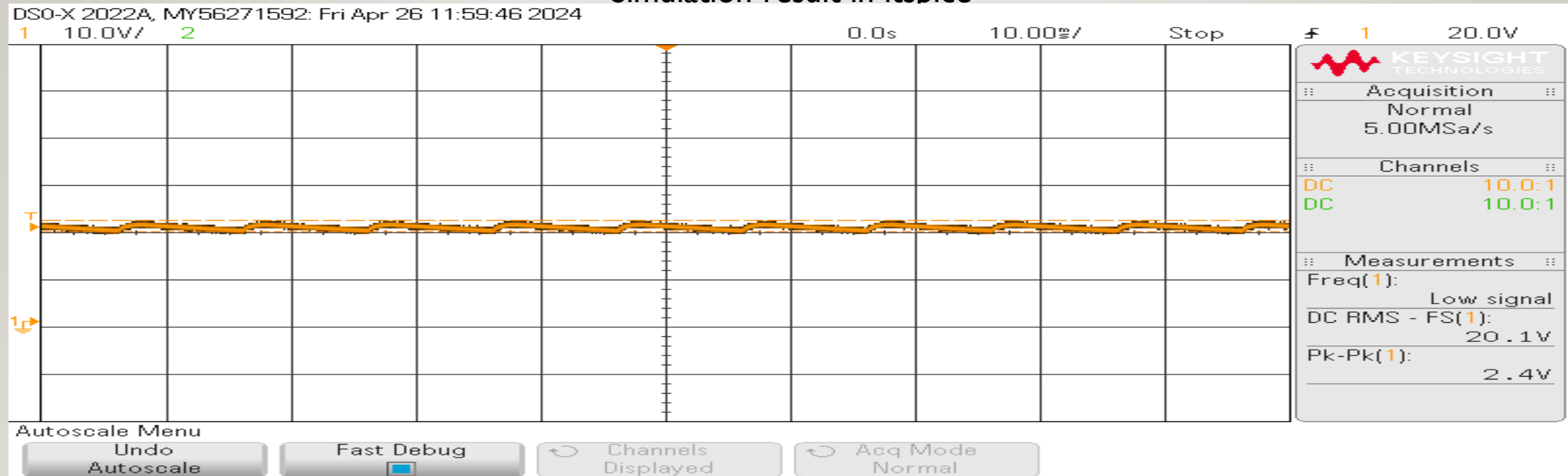

DSO result

CALCULATION

SIMULATION -

$$\text{Ripple (2}\delta\text{V)} = \frac{I}{2fc} = \frac{214 \mu}{2 \times 50 \times 1 \mu} = 2.14 \text{ volt}$$

$$V_{dc} = 21.089 \text{ volts}$$

$$\text{Efficiency} = 93.7\%$$

DSO reading –

$$\text{Ripple (2}\delta\text{V)} = 2.4 \text{ volt}$$

$$V_{dc} = 20 \text{ volt}$$

$$\text{Efficiency} = 88.8\%$$

$$\text{Rectification efficiency} = \frac{V_{dc}}{V_{s,peak}}$$

THANK YOU

